



סדנה מעשית אלקטרוניקה 1

סדנה מעשית באלקטרוניקה, שמטרתה להקנות בסיס של עבודה עם רכיבים אלקטרוניים. הסדנה תועבר על ידי אלדד הלרמן, סטודנט שנה ב' להנדסת חשמל ומדעי המחשב.

מה בתכנון?

- נבנה מחלק מתח.
- נבנה מעגל של נורה וכפתור, ואז נשלב לד צבעוני.
- נציג פעימות לב באמצעות נורה.
- נבנה מעגלי RC ו-RLC ונראה את התנודות.
- נבנה מעגל של נורה וכפתור עם שבב של שער לוגי.
- למתקדמים – עבודה עם שבבים והיכרות עם ה-555.



13.02.2024



16:00 – 19:00




מעבדת הנדסה

קומה מתחת לאודיטוריום

SI prefixesV · T · E

Prefix		Base 10	Decimal	Adoption [nb 1]
Name	Symbol			
quetta	Q	10 ³⁰	1 000 000 000 000 000 000 000 000 000 000 000	2022 ^[1]
ronna	R	10 ²⁷	1 000 000 000 000 000 000 000 000 000 000	
yotta	Y	10 ²⁴	1 000 000 000 000 000 000 000 000 000 000	1991
zetta	Z	10 ²¹	1 000 000 000 000 000 000 000 000 000	
exa	E	10 ¹⁸	1 000 000 000 000 000 000 000 000	1975 ^[2]
peta	P	10 ¹⁵	1 000 000 000 000 000 000 000	
tera	T	10 ¹²	1 000 000 000 000 000 000	1960
<i>giga</i>	G	10 ⁹	1 000 000 000	
<i>mega</i>	M	10 ⁶	1 000 000	1873
<i>kilo</i>	k	10 ³	1 000	
<i>hecto</i>	h	10 ²	100	1795
<i>deca</i>	da	10 ¹	10	
—	—	10 ⁰	1	—
<i>deci</i>	d	10 ^{−1}	0.1	1795
<i>centi</i>	c	10 ^{−2}	0.01	
<i>milli</i>	m	10 ^{−3}	0.001	
<i>micro</i>	μ	10 ^{−6}	0.000 001	1873
<i>nano</i>	n	10 ^{−9}	0.000 000 001	
pico	p	10 ^{−12}	0.000 000 000 001	1960
femto	f	10 ^{−15}	0.000 000 000 000 001	
atto	a	10 ^{−18}	0.000 000 000 000 000 001	1964
zepto	z	10 ^{−21}	0.000 000 000 000 000 000 001	
yocto	y	10 ^{−24}	0.000 000 000 000 000 000 000 001	1991
ronto	r	10 ^{−27}	0.000 000 000 000 000 000 000 000 001	
qecto	q	10 ^{−30}	0.000 000 000 000 000 000 000 000 000 001	2022 ^[1]

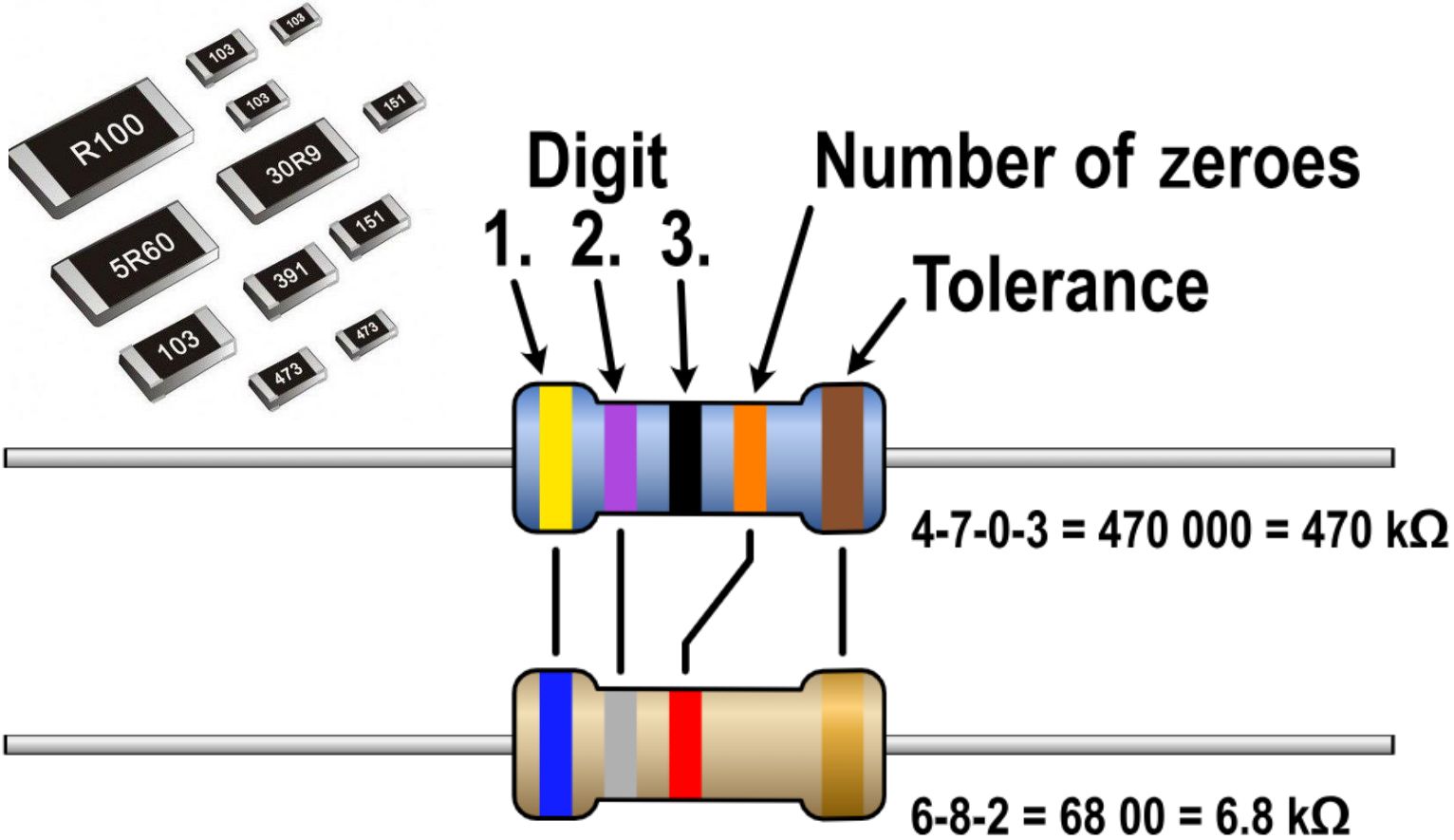

Digit

0

1

2

3

4

5

6

7

8

9

Tolerance

Silver
±10 %

Gold
±5 %

±1 %

±0.5 %

±0.1 %

Resistors



Variable Resistors



Variable



Potentiometer

Switches




SPST



SPDT



SP3T

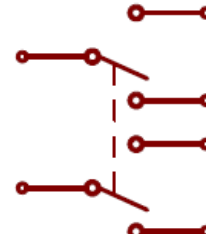

DPDT

Capacitors



Polarized

Inductors



Diodes



LED



Photodiode



Schottky



Zener

Voltage Sources



DC



AC

Batteries




1 cell



2 cells

Voltage Nodes

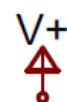

GND



GND









AGND




Arduino™ UNO Reference Design

Reference Designs ARE PROVIDED "AS IS" AND "WITH ALL FAULTS". Arduino DISCLAIMS ALL OTHER WARRANTIES, EXPRESS OR IMPLIED, REGARDING PRODUCTS, INCLUDING BUT NOT LIMITED TO, ANY IMPLIED WARRANTIES OF MERCHANTABILITY OR FITNESS FOR A PARTICULAR PURPOSE


Arduino may make changes to specifications and product descriptions at any time, without notice. The Customer must not rely on the absence or characteristics of any features or instructions marked "reserved" or "undefined." Arduino reserves these for future definition and shall have no responsibility whatsoever for conflicts or incompatibilities arising from future changes to them. The product information on the Web Site or Materials is subject to change without notice. Do not finalize a design with this information.

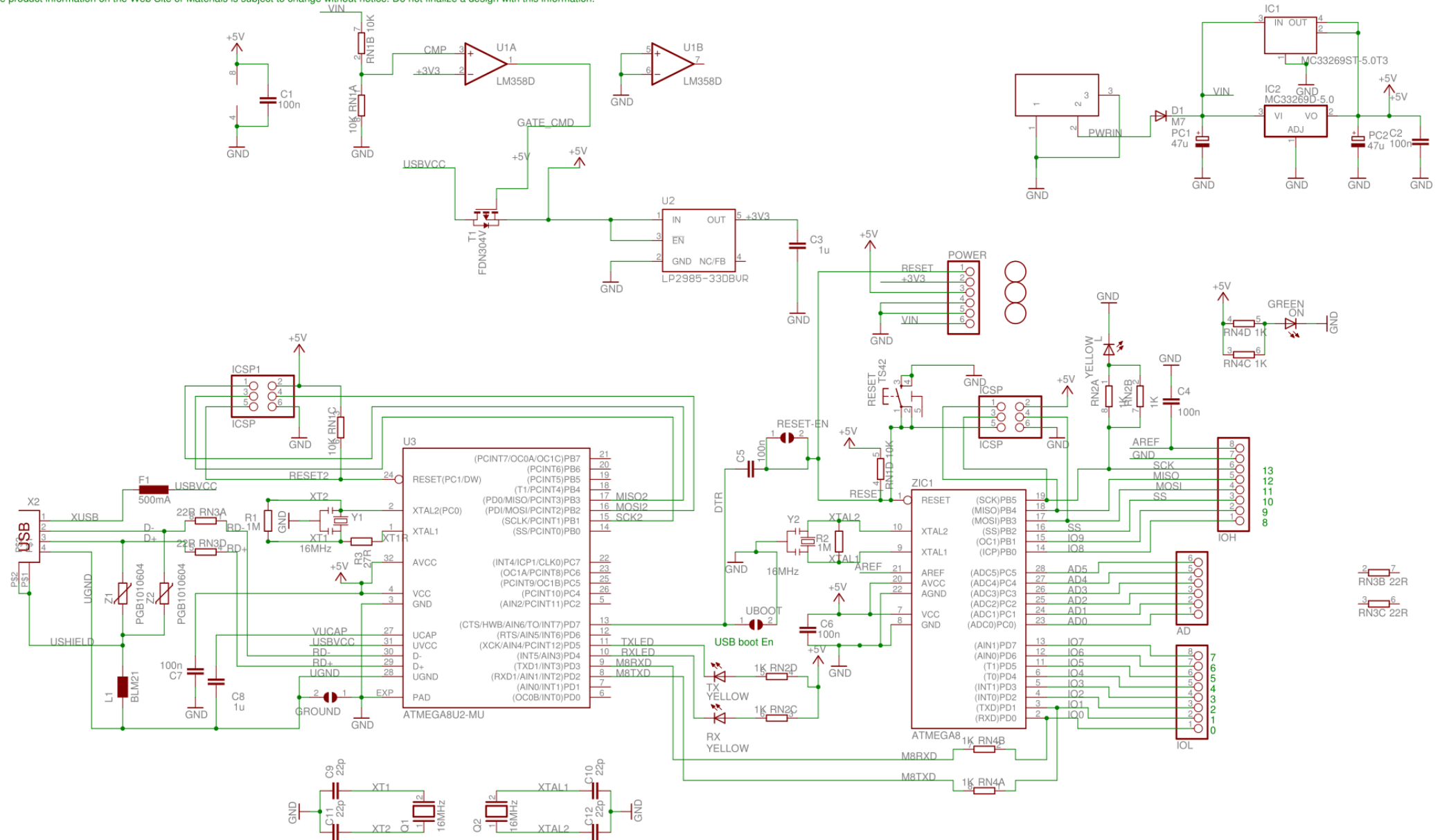

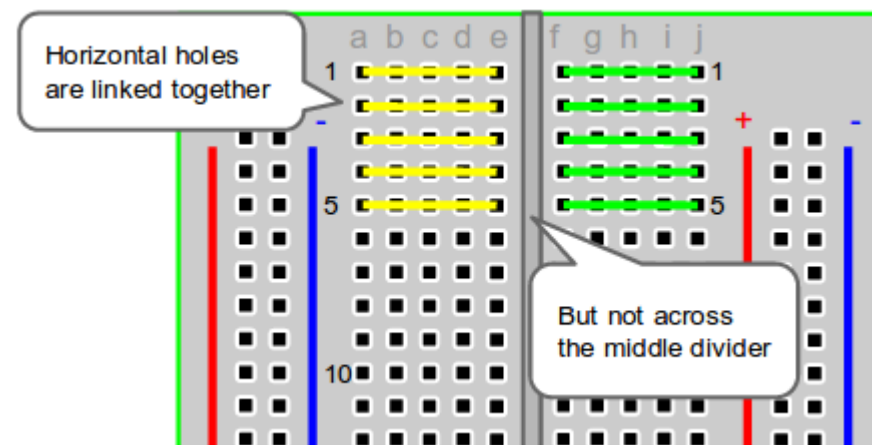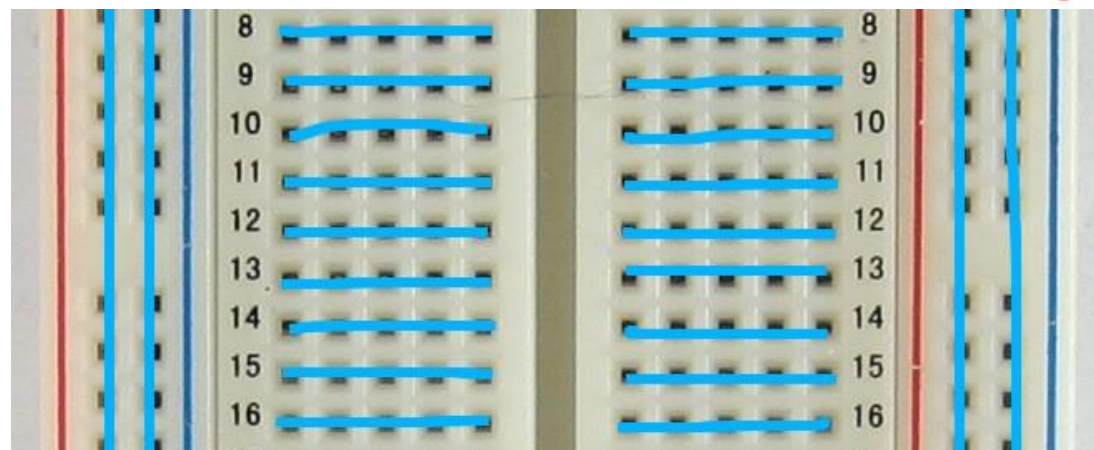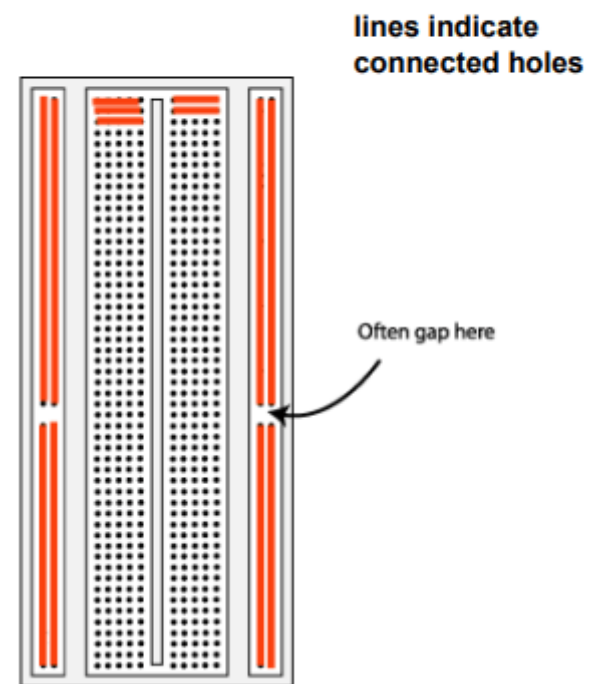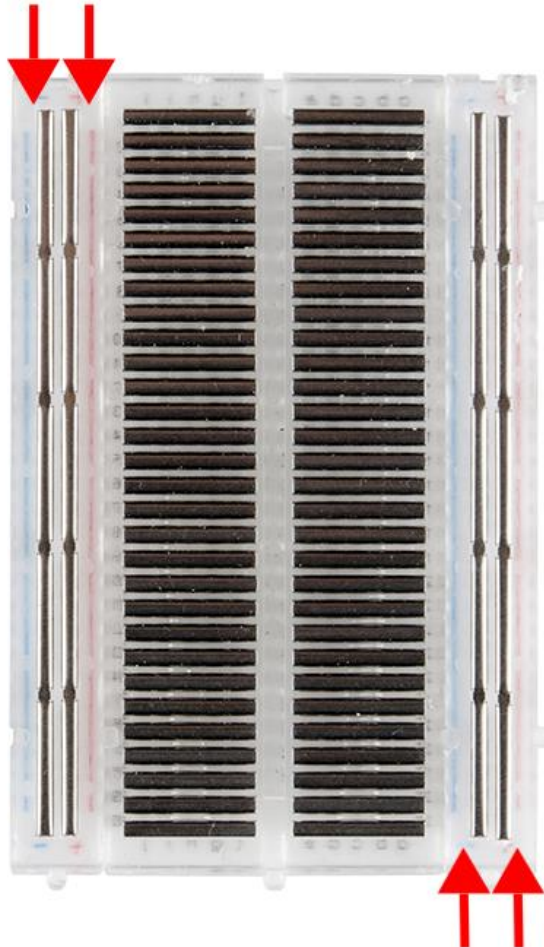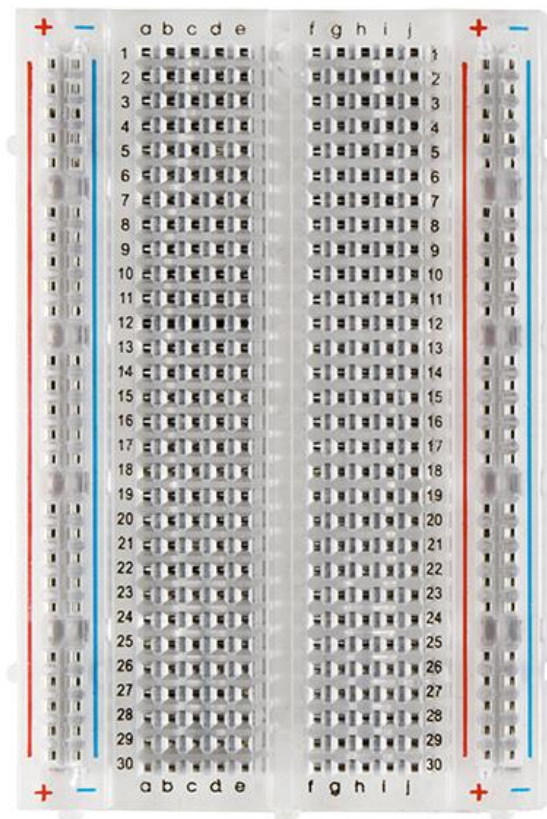


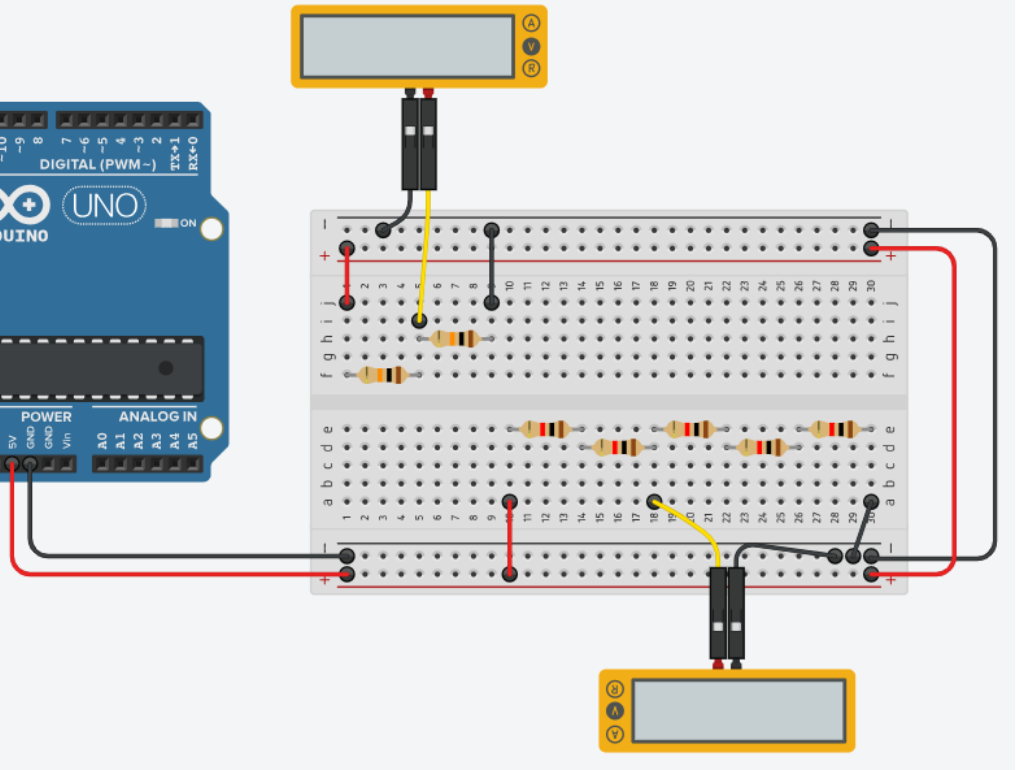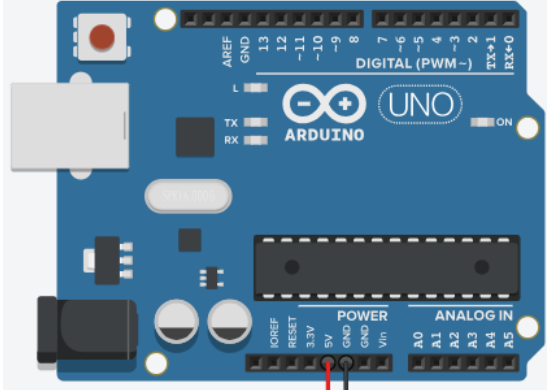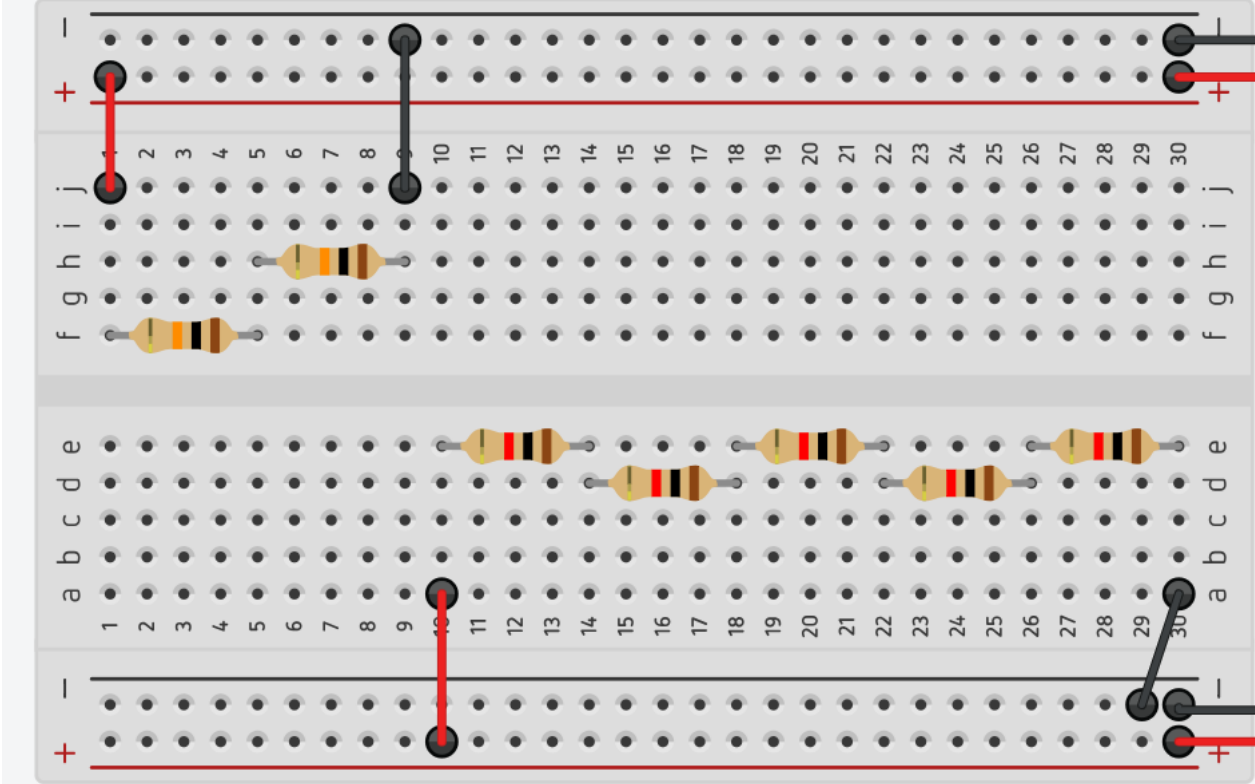


Project #1

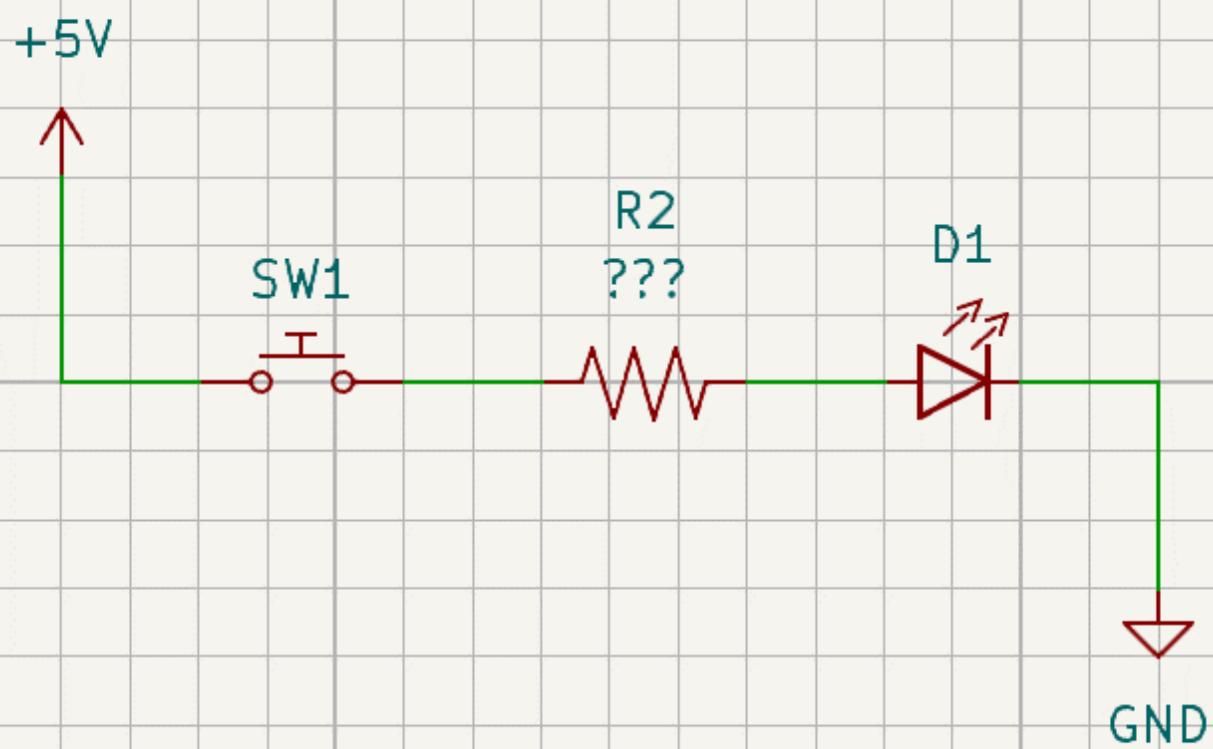


Project #2

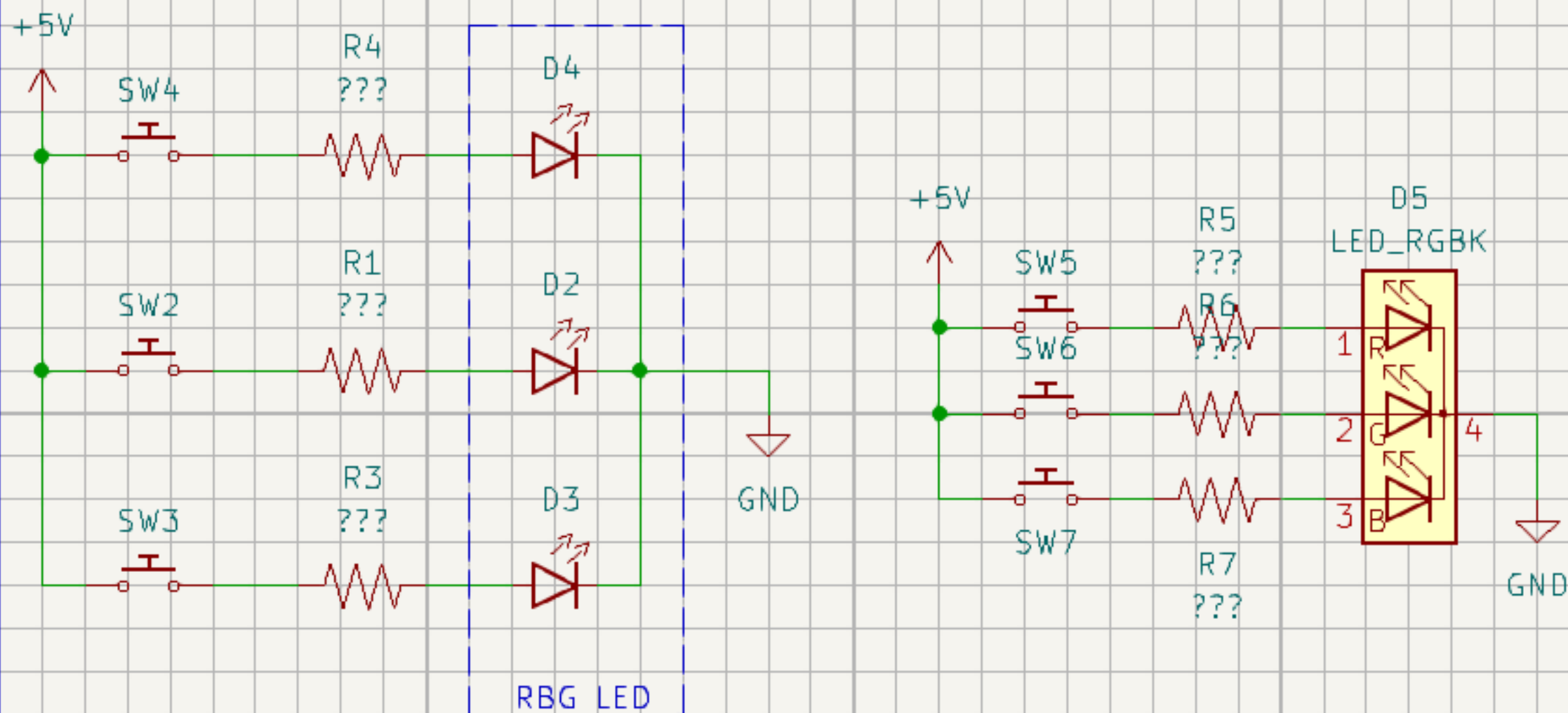


Project #3

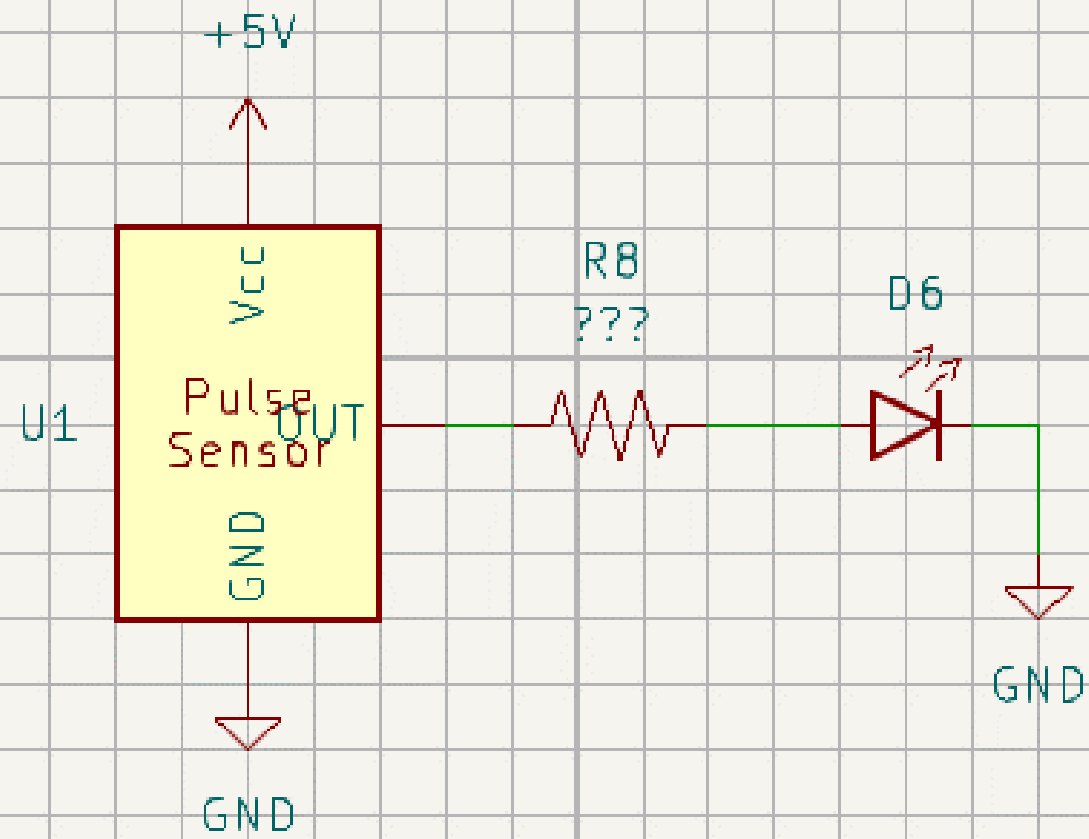



Project #4

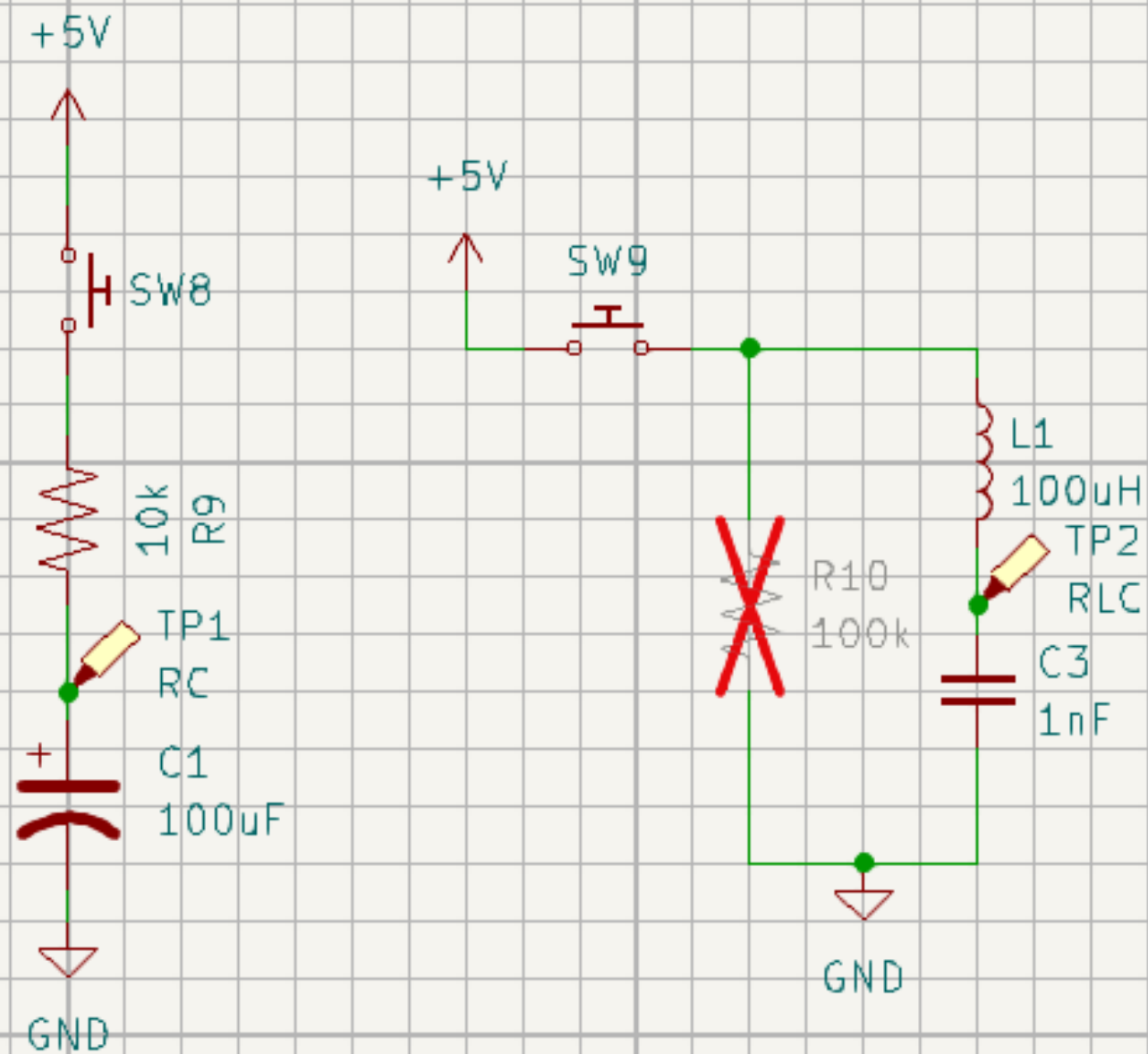




Logic Gates

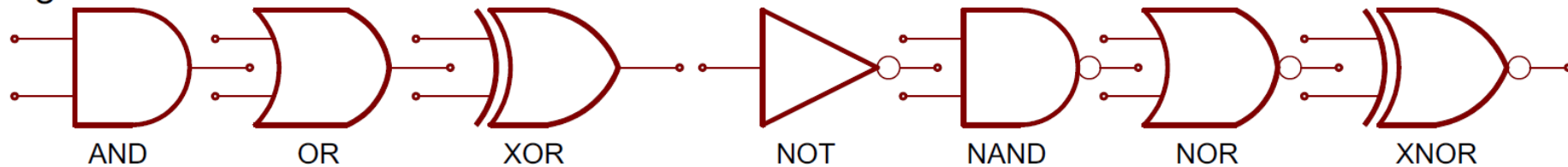


Integrated Circuits

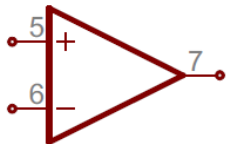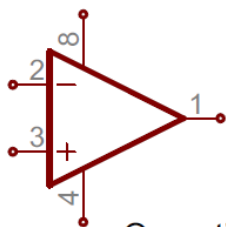


Operational Amplifiers

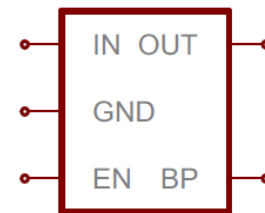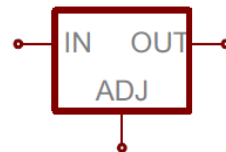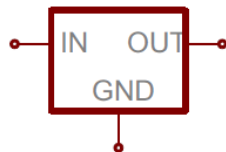



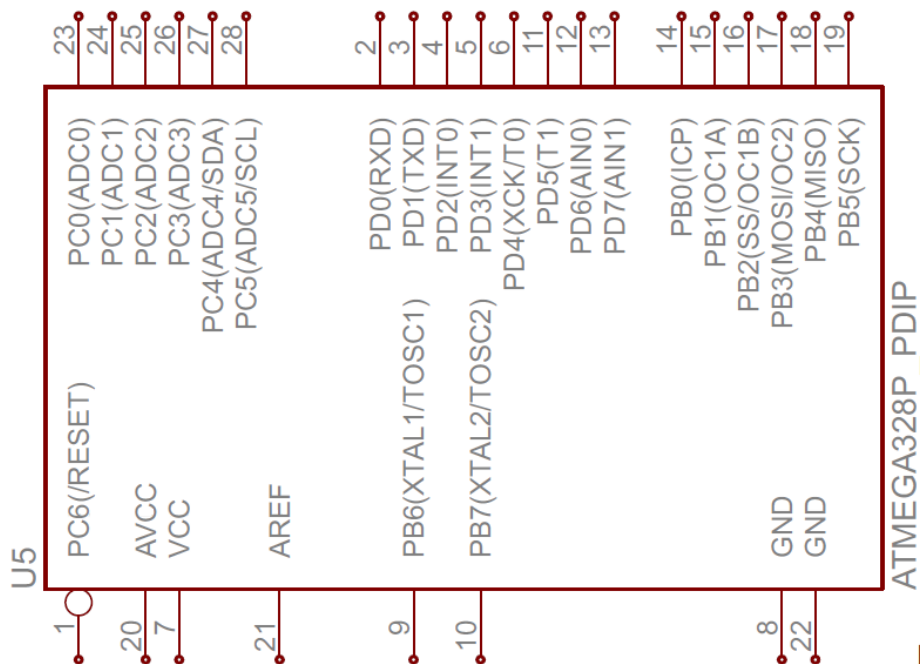

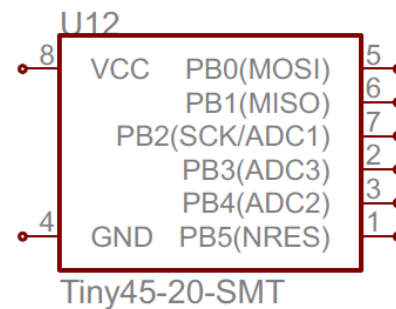


Voltage Regulators




Microcontrollers



Input		Output (Q)						
								
A	B	AND	OR	INH	XOR	NAND	NOR	XNOR
0	0	0	0	0	0	1	1	1
0	1	0	1	0	1	1	0	0
1	0	0	1	1	1	1	0	0
1	1	1	1	0	0	0	0	1

Project #5

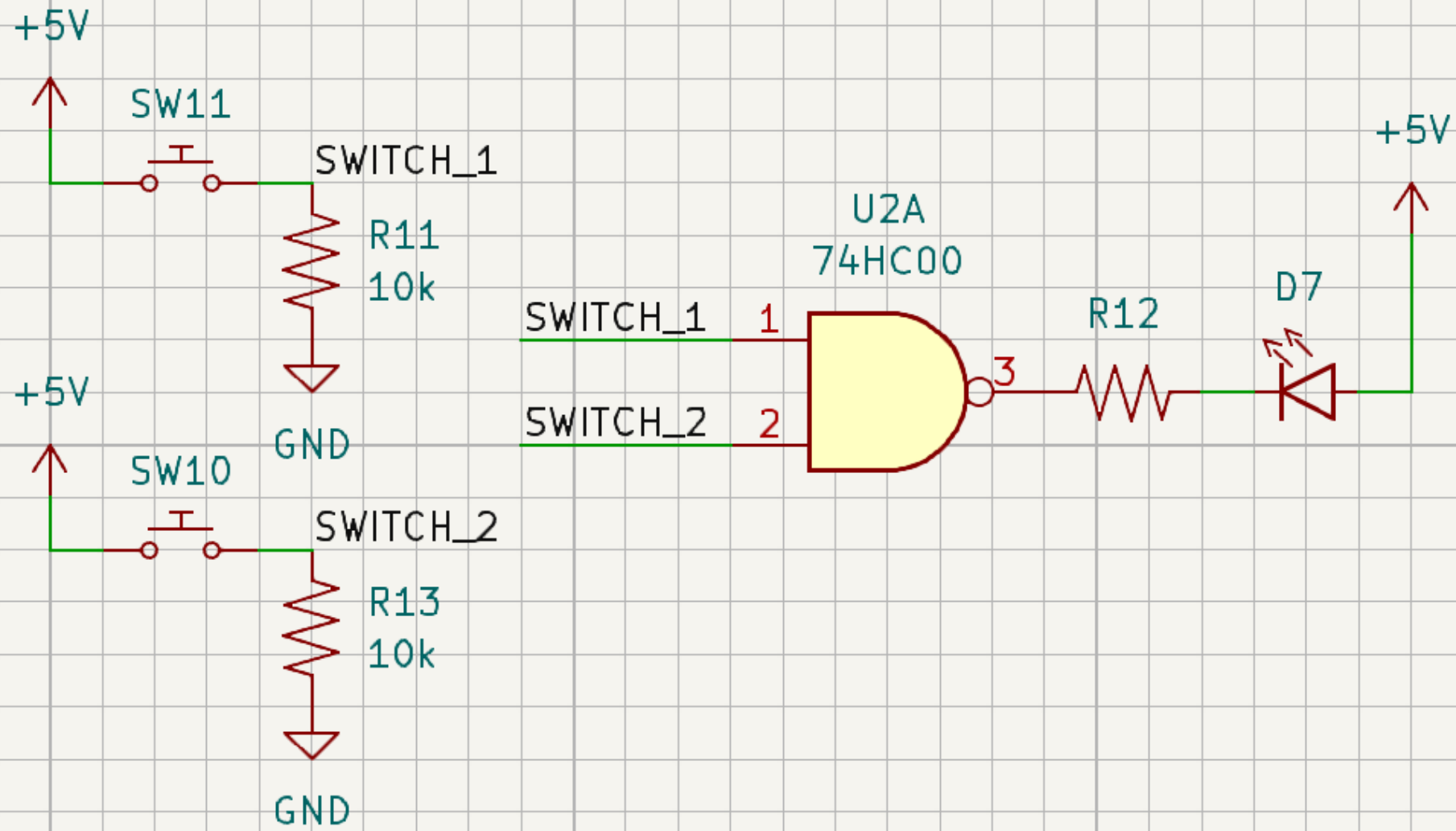

Data taken from 74LS00 datasheet:


5 Pin Configuration and Functions

6.3 Recommended Operating Conditions

over operating free-air temperature range (unless otherwise noted)

		MIN	NOM	MAX	UNIT	
V _{CC}	Supply voltage	SN54xx00	4.5	5	5.5	V
		SN74xx00	4.75	5	5.25	
V _{IH}	High-level input voltage	2			V	
V _{IL}	Low-level input voltage	SNx400, SN7LS400, and SNx4S00			0.8	V
		SN54LS00			0.7	
I _{OH}	High-level output current	SN5400, SN54LS00, and SN74LS00			−0.4	mA
		SNx4S00			−1	
I _{OL}	Low-level output current	SNx400			16	mA
		SN5LS400			4	
		SN7LS400			8	
		SNx4S00			20	

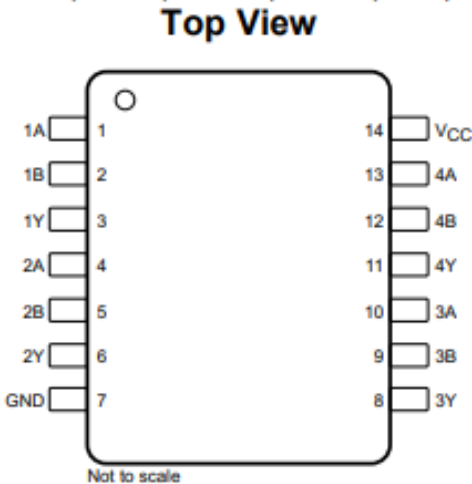0 J, SN54xx00 J and W, SN74x00 D, N, and N;
SN74LS00 D, DB, N, and NS Packages
14-Pin CDIP, CFP, SOIC, PDIP, SO, or SSOP



Logic Diagram, Each Gate (Positive Logic)

